

JNTU ONLINE EXAMINATIONS [Mid 1 - LICA]

1. A typical high gain IC differential amplifier **Has three differential amplifier stages with an open loop gain around 20,00**
2. Difference mode gain A_d of a symmetric emitter coupled differential amplifier is given by **$A_d = 12 h_f R_c R_s + h_i e$**
3. In a difference amplifier, a large R_e leads to increase in **Common-mode gain**
4. The error voltage of an ideal Opamp is **0**
5. One of the Opamps is Norton current differencing Opamp **LM 3900**
6. The output resistance of a 741C Opamp is about **75 Ω**
7. Open loop bandwidth of an Opamp is **5 MHz**
8. Current cannot flow to ground through **A virtual ground**
9. Typical output offset voltage and input offset current of an Opamp are **1 mV, 10 nA**
10. Slew rate of an ideal Opamp is **Infinity**
11. The common mode input is the value of the two inputs **Average**
12. In Opamp compensation techniques are used to **To obtain wider frequency range of operation and avoid instability**
13. Inverting amplifier is also known as **Voltage shunt FB amplifier**
14. For a square wave input, the output of a differentiator will be **Positive & negative spikes**
15. In analog computation we use **Integrator alone but no differentiators**
16. A stable multivibrator has **Two quasi states**
17. The current follower **It is an ideal ammeter, Range is limited by the bias current and output current**
18. In a Monostable multivibrator, if $V_{sat} > V_D$ and $R_1 = R_2$ calculate the time period ($R = 2 k \Omega$ & $C = .002 F$) **2.76**
19. Schmitt Trigger is basically **A bistable multivibrator**
20. A peak detector is an electronic circuit **It tracks the input signal faithfully until it detects a peak and holds until next larger peak value**
21. The gain of a differential amplifier generally falls at the rate of integral multiple of **6 dB per octave**
22. In a differential amplifier, use of a constant current CE amplifier stage in place of emitter resistor R_e causes CMRR **To increase**
23. Which of the following statements is not for a cascade level shifter **It can step up the input voltage**
24. An Operational amplifier is a **High gain direct coupled amplifier**
25. A typical medium gain IC Opamp **Has open loop gain of about 2500**
26. The output stage of an Opamp circuit provides **Low output impedance**
27. Under ideal conditions, for Non-inverting amplifier **R_o = 0**
28. In open loop configuration, the op-amp works in **Linear region**
29. The algebraic difference between the currents into the inverting and non-inverting terminals is known as **Input offset current**
30. PSRR of a good quality Opamp is of the order of **100 dB**
31. 1. An Opamp slew rate limits its output swing at high frequency 2. The bode plot for standard Opamp shows the gain decreasing at 20 dB per decade beyond the break frequency **1 True, 2 True**
32. An example of internally compensated Opamp is **741**
33. In an Opamp inverting amplifier configuration with an input resistance (R_1) and a feedback resistance (R_2), it is normal practice to connect a resistance (R) equal to parallel combination of (R_1) & (R_2) from the non-inverting input to ground. This is done to **Compensate for the effects of input bias currents**
34. The input to an active integrator is 0V. Due to the offset voltage, the output of the integrator will be **Ramp voltage**
35. In all practical Opamp integrators, it is preferable to use the configuration as shown in the Figure 15. In what way does the additional resistance R_1 help Figure 15 **R_1 >> R**
36. The width of the output pulse of a monostable multivibrator is given by **0.69 RC**
37. One of the following statements in reference to voltage follower configuration using Opamp is incorrect **Its input impedance is very high almost approaching its open loop input impedance**
38. In a Astable Multivibrator if $R_1 = R_2$ then the total time period $T = 2RC$

JNTU ONLINE EXAMINATIONS [Mid 1 - LICA]

39. Calculate the Hysteresis voltage for a Schmitt Trigger. $R_1 = 2\text{ k}$, $R_2 = 1\text{ k}$ and $V_s = 15\text{ V}$ **10**
40. In an active peak detector, the discharging time constant is **> time period of the input**
41. A typical high gain IC differential amplifier **Has power dissipation of about 100 micro watts**
42. Differential transconductance gm of differential amplifier equals (Where I_C is the collector current of the CE stage in the emitter circuit of the differential amplifier) **102 V/I**
43. A cascade amplifier uses **Two stages of CE amplifier**
44. Indicate the false statement with reference to Opamp **The differential gain is 0 dB at unity gain crossover frequency**
45. Opamp is also known as current differencing Opamp **Isolation Opamp**
46. The output resistance of a 741C Opamp is about **200 Ω**
47. Open loop bandwidth of an Opamp is **5 GHz**
48. The loop gain βA **May not equal to 1**
49. The input bias current of 741C Opamp is about **500 nA**
50. The slew rate of an Opamp is given by **-ΔV/A = MAX**
51. The CMRR is a problem for **Both inverting & non inverting configuration**
52. For an ideal op-amp the bandwidth is **Zero**
53. In an inverting amplifier, $R_1 = 5\text{ k}$; $R_f = 50\text{ k}$ & $V_i = 2\text{ V}$, calculate the V_o . **-15\text{ V}**
54. What will be the output in case of integrator **-t / 0.01**
55. The number of op-amps required to perform addition & subtraction simultaneously **1**
56. What is the basic element in instrumentation amplifier? **Transistor**
57. The Opamp circuit shown below in Figure 17 is a **Voltage follower**
58. In case of a stable circuit, if $R_1 = 1.16 R_2$ the expression for time period will be **$T = 3RC$**
59. Calculate the Hysteresis voltage for a Schmitt Trigger. $R_1 = 2\text{ k}$, $R_2 = 1\text{ k}$ and $V_s = 15\text{ V}$ **14**
60. In case of log amplifier circuit the temperature compensation is provided by using element. **Transistor**
61. Most of the linear ICs are based on the two transistor differential amplifier because of its **High CMRR**
62. The differential gain of an Opamp should be **Very large**
63. Which of the following specifications is not specified for a difference amplifier? **Common-mode current range**
64. In basic comparator consists of **Opamp used in open loop**
65. is the important parameter of the Opamp, when used in sample and hold circuit and digital to analogue converter **Settling time**
66. The following property of Opamp permits voltage gain down to zero of frequency **High open loop gain**
67. In the ideal transfer curve of Opamp the output voltage is proportional to the difference of the input voltages until it reaches saturation and thereafter the output **Directly remains constant**
68. The virtual ground **Acts like short for voltage and does not drive any current to the ground**
69. The input bias current of 741C Opamp is about **500 nA**
70. The slew rate of an Opamp is given by **-ΔV/A = MAX**
71. An Opamp has a gain of 50 and bandwidth of 100 KHz. Its unity gain frequency is **5 MHz**
72. For an ideal op-amp the bandwidth is **Infinity**
73. In an inverting Opamp $Z_i = 22\text{ kΩ}$, $Z_f = 68\text{ kΩ}$ and $V_i = +0.5\text{ V P-P}$. The output voltage will be approximately **-1.5\text{ V P-P}**
74. The Opamp differentiator **Is inherently unstable and can be stabilized by connecting a resistor in series with the capacitor**
75. What is the voltage gain of circuit shown in Figure 15 Figure 15 **$V_b - V_a$**
76. In a multivibrator, **When one transistor is on, the other is off**
77. One of the following statements in reference to voltage follower configuration using Opamp

JNTU ONLINE EXAMINATIONS [Mid 1 - LICA]

pis incorrect Its input impedance is very high almost approaching its open loop input impedance because of magnitude

78. Circuit used for production of delay is A monostable multivibrator

79. Schmitt trigger circuit employs feedback method. Positive

80. The Peak Detector circuit stores the following values higher new value

81. Most of the linear ICs are based on the two transistor differential amplifier because of its High CMRR

82. The differential gain of the an Op amp should be Very large

83. The level translator stage is used for To shift the output dc level down to zero

84. In basic comparator consists of Opamp used in open loop

85. A typical medium gain IC Opamp Has open loop gain of about 2500

86. The output stage of an Opamp circuit provides Low output impedance

87. An ideal Opamp is used to make an inverting amplifier. The two input terminals of the Opamp are at the same potential because CMRR is infinity, open loop gain of the op-amp is infinity

88. One of the inputs of an Opamp is open. The output voltage will be 0

89. The input offset current of 741C Opamp has maximum value of about 200 nA

90. PSR is expressed as µV/V

91. X is the gain bandwidth product of the inverting amplifier and z is the gain bandwidth product of the non inverting amplifier. Then $X = Z R_2 R_1 + R_2$

92. The drift is minimized by Offset trimming

93. A non inverting Opamp has $Z_i = 10 \text{ k}\Omega$, feedback resistor $R_f = 120 \text{ k}\Omega$ and $V_i = +0.6 \text{ V P-P}$. The output voltage is +7.8 \text{ V P-P}

94. The integrator will have a DC gain Equal to open loop gain

95. In case of non inverting summing amplifier to get $V_o = V_1 + V_2 + V_3$ the condition is All resistances must be half the R_f

96. The Opamp below has $A_v = 20,000$ and $Z_o = 20\Omega$. The approximate output voltage V_o is given by Figure 16 Figure 16 2V

97. Will it be true to say that the input impedance of an Opamp voltage follower would always decrease with increase in frequency. Yes, it is true dependent on current

98. In a Astable Multivibrator if $R_1 = R_2$ then the total time period $T = 2RC$

99. Calculate the Hysteresis voltage for a Schmitt Trigger. $R_1 = 2k$, $R_2 = 1k$ and $V_s = 15 \text{ V}$ 10

100. The Opamp in an active half wave rectifier has a gain of 200,000. The closed loop voltage is 3.5 µV

101. Most of the linear ICs are based on the two transistor differential amplifier because of its High CMRR

102. In a differential amplifier, use of a constant current CE amplifier stage instead of emitter coupled resistor resistor causes CMRR To increase

103. The level translator stage is used for To shift the output dc level down to zero

104. The error voltage of an ideal Opamp is 0

105. An ideal Opamp with a very high input impedance, very large CMRR and extremely low values of offset and offset drifts Norton Opamp

106. A good quality Opamp has high selectivity

107. An ideal Opamp is used to make an inverting amplifier. The two input terminals of the Opamp are at the same potential because The open loop gain of the op-amp is infinity

108. A practical Opamp has Finite gain and infinite input resistance

109. While making measurement with an Opamp, it was observed that the current flowing to a

JNTU ONLINE EXAMINATIONS [Mid 1 - LICA]

rd sinverting and non inverting inputs were $4\mu A$ and $2\mu A$ respectively. The input offset current in the case would be **$4\mu A$**

11.0. The Slew rate calculation depends on only. **Input**

11.1. An Op amp has a gain of 50 and bandwidth of 100 KHz. Its unity gain frequency is **5 MHz**

11.2. The drift is minimized by **Offset leveling**

11.3. A non inverting Op amp has $Z_i = 10\text{ k}\Omega$, feedback resistor $R_f = 120\text{ k}\Omega$ and $V_i = +0.6\text{ V}$ P-T

he output voltage **-7.8 V P-P**

11.4. The input signal will be differentiated properly if the time period T of the input signal is **$T \leq R_f C_1$**

11.5. In case of non inverting summing amplifier to get $V_o = V_1 + V_2 + V_3$ the condition is **All resistances are same**

11.6. The Op amp circuit given below Figure 16 behaves as Figure 16 **Scale changer**

11.7. Will it be true to say that the input impedance of an Op amp voltage follower would always decrease with increase in frequency **Input impedance of a voltage follower is dependent on current**

11.8. In a Astable Multivibrator if $R_1 = R_2$ then the total time period $T = \frac{3}{2}C$

11.9. Calculate the Hysteresis voltage for a Schmitt Trigger. $R_1 = 2\text{ k}$, $R_2 = 1\text{ k}$ and V_s at = **15 v** **1.2**

12.0. The Op amp in an active half wave rectifier has a gain of 200,000. The closed loop voltage is **3.5\mu V**

12.1. A typical high gain IC differential amplifier

Has three differential amplifier stages with an open loop gain around 20,000

12.2. In a differential amplifier the differential input resistance R_i equals **2 kie**

12.3. A differential amplifier consists of **Two input terminals and two output terminals**

12.4. A differential amplifier having an open loop gain of 80 dB was fed with 2 mV DC at non invert

ing input and 1.9 mV DC at inverting input. The output will be **1 VDC**

12.5. is the important parameter of the Opamp, when used in sample and hold circuit and digital to analogue converter **Settling time**

12.6. An Op amp having an open loop differential gain of 110 dB and a CMRR rating of 100dB will have an open loop common mode gain of **10 dB**

12.7. The CMRR of a good quality Opamp of the order of **120 dB**

12.8. The loop gain **B** **A** **May not equal to 1**

12.9. The input offset current of 741 Opamp has maximum value of about **200 nA**

13.0. Slew rate of typical Opamp is of the order of **20V/\mu s**

13.1. Full power bandwidth of an Opamp **Is the maximum frequency up to which full output voltage swing can be obtained**

13.2. For an ideal op-amp the bandwidth is **infinity**

13.3. Inverting amplifier is also known as **Voltage shunt FB amplifier**

13.4. The variation of the output of an Opamp integrator with time due to offsets is given by $dV_O/dt = dV_O/R_C + dI_B/C$

13.5. In case of inverting summing amplifier if $R_1 = R_2 = R_3 = 3R_f$ then V_o is **$V_1 + V_2 + V_3/3$**

13.6. The frequency of oscillation in case of an astable multivibrator depends mainly on

(a) RC values of the circuit

13.7. The Opamp circuit shown below in Figure 17 is a Figure 17 **Voltage follower**

13.8. A comparator **Compares the voltage levels of two signals**

13.9. Calculate the Hysteresis voltage for a Schmitt Trigger. $R_1 = 2\text{ k}$, $R_2 = 1\text{ k}$ and V_s at = **15 v** **10**

JNTU ONLINE EXAMINATIONS [Mid 1 - LICA]

140. Log amplifiers are used in Analoguedata compression, computation and transducer linearization
141. The differential amplifier gain and the input resistance of a dual input balanced output differential is given by $R_c/re, 2Bacre$
142. The differential gain of the an Op amp should be Very large
143. Topologically, a difference amplifier corresponds to a TTL OR gate
144. In basic comparator consists of Opamp used in open loop
145. Opamp is also known as current differencing Opamp Norton Opamp
146. A op-amp is VCVS
147. The ideal value of CMRR is ∞
148. Current cannot flow to ground through A virtual ground
149. Which characteristic is not belonging to D.C characteristics? Slew rate
150. PSRR of a good quality Opamp is of the order of 100 dB
151. X is the gain bandwidth product of the inverting amplifier and z is the gain bandwidth product of the non-inverting amplifier. Then $X = ZR_2 R_1 + R_2$
152. At the crossing frequency or unity, the voltage gain is R_C/re
153. In an Opamp inverting amplifier configuration with an input resistance (R_1) and a feed back resistance (R_2), it is normal practice to connect a resistance (R) equal to parallel combination of (R_1) & (R_2) from the non-inverting input to ground. This is done to Compensate for the effects of input bias currents
154. The variation of the output of an Opamp integrator with time due to offsets is given by dV_0
 $dt = \frac{dV_0}{RC + DiBc}$
155. In the circuit shown in the Figure 15 expression for $I_O/I_i =$ Figure 15 $1 + (R_f/R_i)$
156. The Opamp shown in Figure 16 has $Z_i = 10 M\Omega$, $Z_o = 20\Omega$, $A_v = 20,000$ output voltage is given by Figure 16 20V
157. Will it be true to say that the input impedance of an Opamp voltage follower would always decrease with increase in frequency? Yes, it is true
158. In a Monostable multivibrator, if $V_{sat} >> V_D$ and $R_1 = R_2$ calculate the time period ($R = 2k$ & $C = .002F$) 2.76
159. Calculate the Hysteresis voltage for a Schmitt Trigger. $R_1 = 2k$, $R_2 = 1k$ and $V_{sat} = 15V$ 10
160. The circuit shown below in Figure 20 can be used as a Figure 20 Logarithmic amplifier
161. Most of the linear ICs are based on the two transistor differential amplifier because of its Input voltage dependent linear transfer characteristics
162. The ability of differential amplifier to reject a common mode signal is called Common mode rejection ratio
163. In a differential amplifier, use of a constant current CE amplifier stage in place of emitter coupled circuit resistor results in very high value of CMRR
164. An Operational amplifier is a High gain CE amplifier
165. Which out of the following IC Opamps has the best tolerance and minimum cost 709C
166. With reference to the power supply of an Opamp Current always flows into the V+ terminal and flows out of the V- terminal uses dual power supply
167. Openloop bandwidth of an Opamp is 5KHz
168. Current cannot flow to ground through A mechanical ground
169. Currents that flow in the input leads of an Op-amp Are required to support the collector current and are known as bias currents
170. A general purpose Opamp has a PSRR rating of 100dB. This implies that at a 1V change in the p

JNTU ONLINE EXAMINATIONS [Mid 1 - LICA]

power supply will produce an input offset voltage change of **10 μV**

171. Let the magnitude of the gain in the inverting Op amp circuit shown in the Figure 11 be **X** with switch S1 open when S1 is closed the magnitude of gain becomes **Figure 11 - X**

172. At the crossing frequency or unity, the voltage gain is **0**

173. In an Op amp inverting amplifier configuration with an input resistance (R_1) and a feed back resistance (R_2), it is normal practice to connect a resistance (R) equal to parallel combination of (R_1) & (R_2) from the non-inverting input to ground. This is done to **Compensate for the effects of input offset voltage**

174. The Op amp differentiator **Is inherently unstable**

175. In case of inverting summing amplifier if $R_1 = R_2 = R_3 = R_f$ then V_o is **$V_o = -V_i$**
 $1 + V_2 + V_3$

176. The width of the output pulse of a monostable multivibrator is given by **$0.69 RC$**

177. The current follower **Range is limited by the output current capability at high end**

178. A comparator **Compares the voltage levels of two signals**

179. Schmitt Trigger is basically **An stable multivibrator**

180. The circuit shown below in Figure 20 can be used as a **Figure 20 Logarithmic amplifier**

181. The frequency in which differential gain in Op amp is zero dB is known as **Unity gain cross over frequency**

182. The tail of a differential amplifier acts like a **Battery**

183. Which of the following specifications is not specified for a difference amplifier?
Common-mode current range

184. A differential amplifier having an open loop gain of 80 dB was fed with 2 mV DC at non inverting input and 1.9 mV DC at inverting input. The output will be **1 VDC**

185. Op amp is also known as current differencing Op amp **Norton Op amp**

186. With reference to the power supply of an Op amp

Current always flows into the V+ terminal and flows out of the V-terminal uses dual power supply

187. The gain of an Op amp is nearly **10⁵**

188. The loop gain βA **May not equal to 1**

189. The input offset current of 741 Op amp has maximum value of about **200 nA**

190. For defining the slew rate type of input signal is used. **Square wave**

191. The gain-bandwidth product of 741 Op amp is about **1 MHz**

192. In dominant pole compensation, the modified loop gain drops to 0 dB

With a slope of -20 dB/decade at the first break frequency of the uncompensated amplifier

193. A non inverting Op amp has $Z_i = 10 \text{ k}\Omega$, feedback resistor $R_f = 120 \text{ k}\Omega$ and $V_i = +0.6 \text{ VP-P}$. The output voltage is **+7.8 \text{ VP-P}**

194. The input signal will be differentiated properly if the time period T of the input signal is **$T \geq R_f C_1$**

195. The given Figure 15 Op amp has voltage gain of 200,000. The input Miller Capacitance is F

Figure 15 **$1 + (R_f / R)$**

196. The functionality of Resistive Transducer used in case of Instrumentation amplifier is the

resistance changes with **Temperature**

197. The input impedance of a current follower is **Ideally zero**

198. In case of a Comparator, the op-amp output will be operated in region. **Saturation**

199. In a Schmitt Trigger the Upper Threshold Voltage is given by **$[R_1 / (R_1 + R_2)] (+V_{sat})$**

200. Log amplifiers are used in **Analoguedata compression, computation and transducer linearization**